
Lecture 16: Instruction Level Parallelism

-- Dynamic Scheduling (OOO) via Tomasulo's Approach

CSCE 513 Computer Architecture

Department of Computer Science and Engineering

Yonghong Yan

yanyh@cse.sc.edu

<https://passlab.github.io/CSCE513>

Topics for Instruction Level Parallelism

- 5-stage Pipeline Extension, ILP Introduction, Compiler Techniques, and Branch Prediction
 - C.5, C.6
 - 3.1, 3.2
 - ~~Branch Prediction, C.2, 3.3~~
- Dynamic Scheduling (OOO)
 - 3.4, 3.5
- Hardware Speculation and Static Superscalar/VLIW
 - 3.6, 3.7
- Dynamic Superscalar, Advanced Techniques, ARM Cortex-A53, and Intel Core i7
 - 3.8, 3.9, 3.12
- SMT: Exploiting Thread-Level Parallelism to Improve Uniprocessor Throughput
 - 3.11

Acknowledge and Copyright

- Slides adapted from
 - UC Berkeley course “Computer Science 252: Graduate Computer Architecture” of David E. Culler Copyright(C) 2005 UCB
 - UC Berkeley course Computer Science 252, Graduate Computer Architecture Spring 2012 of John Kubiatowicz Copyright(C) 2012 UCB
 - Computer Science 152: Computer Architecture and Engineering, Spring 2016 by Dr. George Michelogiannakis from UC Berkeley
- <https://passlab.github.io/CSCE513/copyrightack.html>

3.4 Overcoming Data Hazards With Dynamic Scheduling

- **Data Hazards**
- **Control Hazards**

Types of Data Hazards

Consider executing a sequence of

$$r_k \leq r_i \text{ op } r_j$$

type of instructions

Data-dependence

$$\begin{array}{l} r_3 \leq r_1 \text{ op } r_2 \\ r_5 \leq r_3 \text{ op } r_4 \end{array}$$

**Read-after-Write
(RAW) hazard**

Anti-dependence

$$\begin{array}{l} r_3 \leq r_1 \text{ op } r_2 \\ r_1 \leq r_4 \text{ op } r_5 \end{array}$$

**Write-after-Read
(WAR) hazard**

Output-dependence

$$\begin{array}{l} r_3 \leq r_1 \text{ op } r_2 \\ r_3 \leq r_6 \text{ op } r_7 \end{array}$$

**Write-after-Write
(WAW) hazard**

Register vs. Memory Dependence

Data hazards due to register operands can be determined at the decode stage, but data hazards due to memory operands can be determined only after computing the effective address


Store: $M[r1 + \text{disp1}] \leq r2$

Load: $r3 \leq M[r4 + \text{disp2}]$

Does $(r1 + \text{disp1}) = (r4 + \text{disp2})$?


Data Hazards: An Example

I_1	FDIV.D
I_2	FLD
I_3	FMUL.D
I_4	FDIV.D
I_5	FSUB.D
I_6	FADD.D

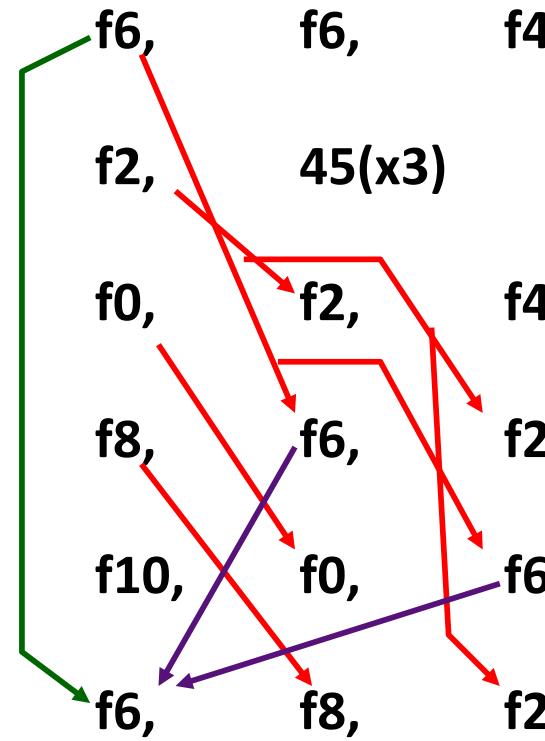

RAW Hazards
WAR Hazards
WAW Hazards

Instruction Scheduling

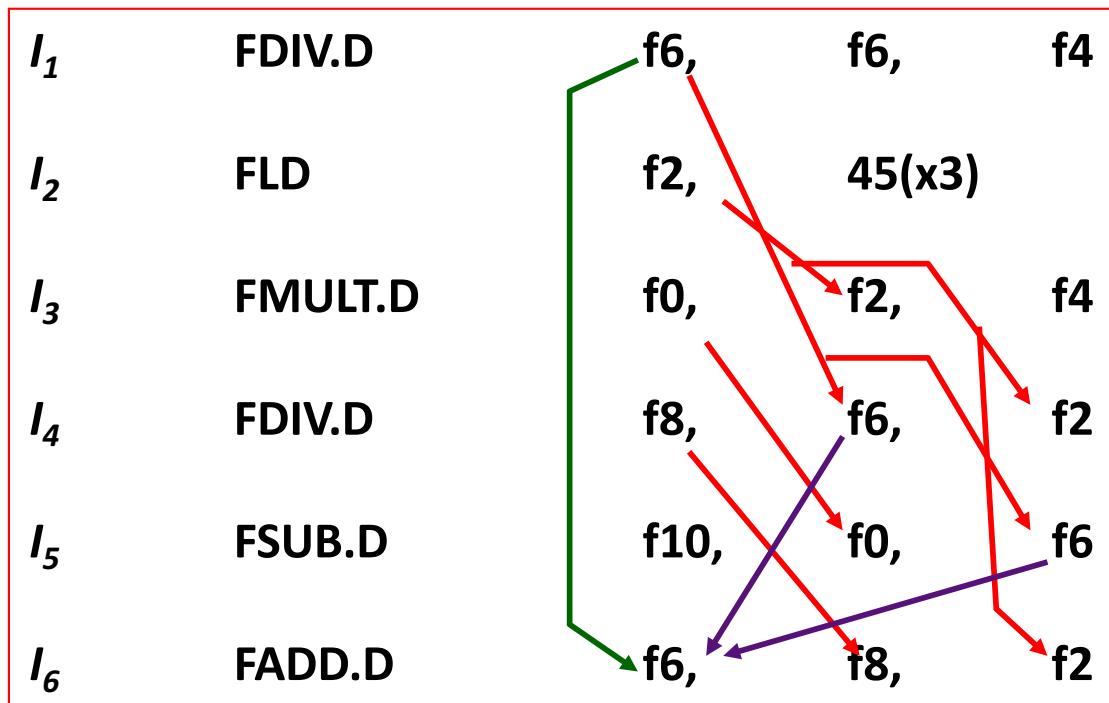


Valid orderings:

in-order I_1 I_2 I_3 I_4 I_5

out-of-order I_2 I_1 I_3 I_4 I_5

out-of-order I_1 I_2 I_3 I_5 I_4

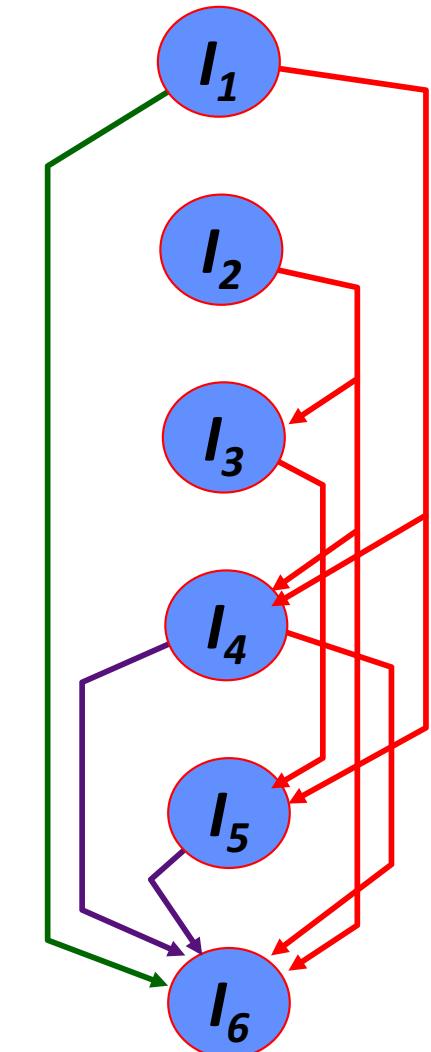

Out-of-order Completion

In-order Issue

						<i>Latency</i>
I_1	FDIV.D	f6,	f6,	f4		4
I_2	FLD	f2,	45(x3)			1
I_3	FMULT.D	f0,	f2,	f4		3
I_4	FDIV.D	f8,	f6,	f2		4
I_5	FSUB.D	f10,	f0,	f6		1
I_6	FADD.D	f6,	f8,	f2		1
<i>in-order comp</i>		1 2	<u>1</u> <u>2</u> 3 4	<u>3</u> 5 <u>4</u> 6 <u>5</u> <u>6</u>		
<i>out-of-order comp</i>		1 2 <u>2</u> 3 <u>1</u> 4 3 5 <u>5</u> 4 6 <u>6</u>				

Underlines are completes

Register Renaming to Eliminate WAR and WAW Hazards


- Example:

DIV.D	F0,F2,F4	Anti-dependence (WAR) on F8
ADD.D	F6,F0,F8	Also on F6 between S.D and MUL.D
S.D	F6,0(R1)	
SUB.D	F8,F10,F14	Output dependence (WAW) on F6
MUL.D	F6,F10,F8	

+ name dependence with F6 and F8

No real data sharing between two instructions.

Register Renaming

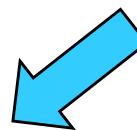▪ Example:	DIV.D	F0,F2,F4
	ADD.D	F6,F0,F8
DIV.D	F0,F2,F4	
ADD.D	F6,F0,F8	S.D
S.D	F6,0(R1)	SUB.D
SUB.D	T2,F10,F14	MUL.D
MUL.D	T1,F10,T2	

- Now only RAW hazards remain, which can be strictly ordered


Dynamic Scheduling

- Rearrange order of instructions to reduce stalls while maintaining data flow
 - *Minimize impacts by RAW Hazards*
 - *Minimize WAW and WAR hazards via Register Renaming*
 - Between registers and memory hazards
- Advantages:
 - Compiler doesn't need to have knowledge of microarchitecture
 - Handles cases where dependencies are unknown at compile time
- Disadvantages:
 - Substantial increase in hardware complexity
 - Complicates exceptions

Dynamic Scheduling

- **Dynamic scheduling implies:**
 - Out-of-order execution
 - Out-of-order completion
- **May create more WAR and WAW hazards**
 - Since execution are out-of-order
- **Scoreboard: C.6**
 - CDC6600 in 1963
- **Tomasulo's Approach**
 - Tracks when operands are available
 - Introduces register renaming in hardware
 - » Minimizes WAW and WAR hazards

Scoreboard Architecture (CDC 6600)

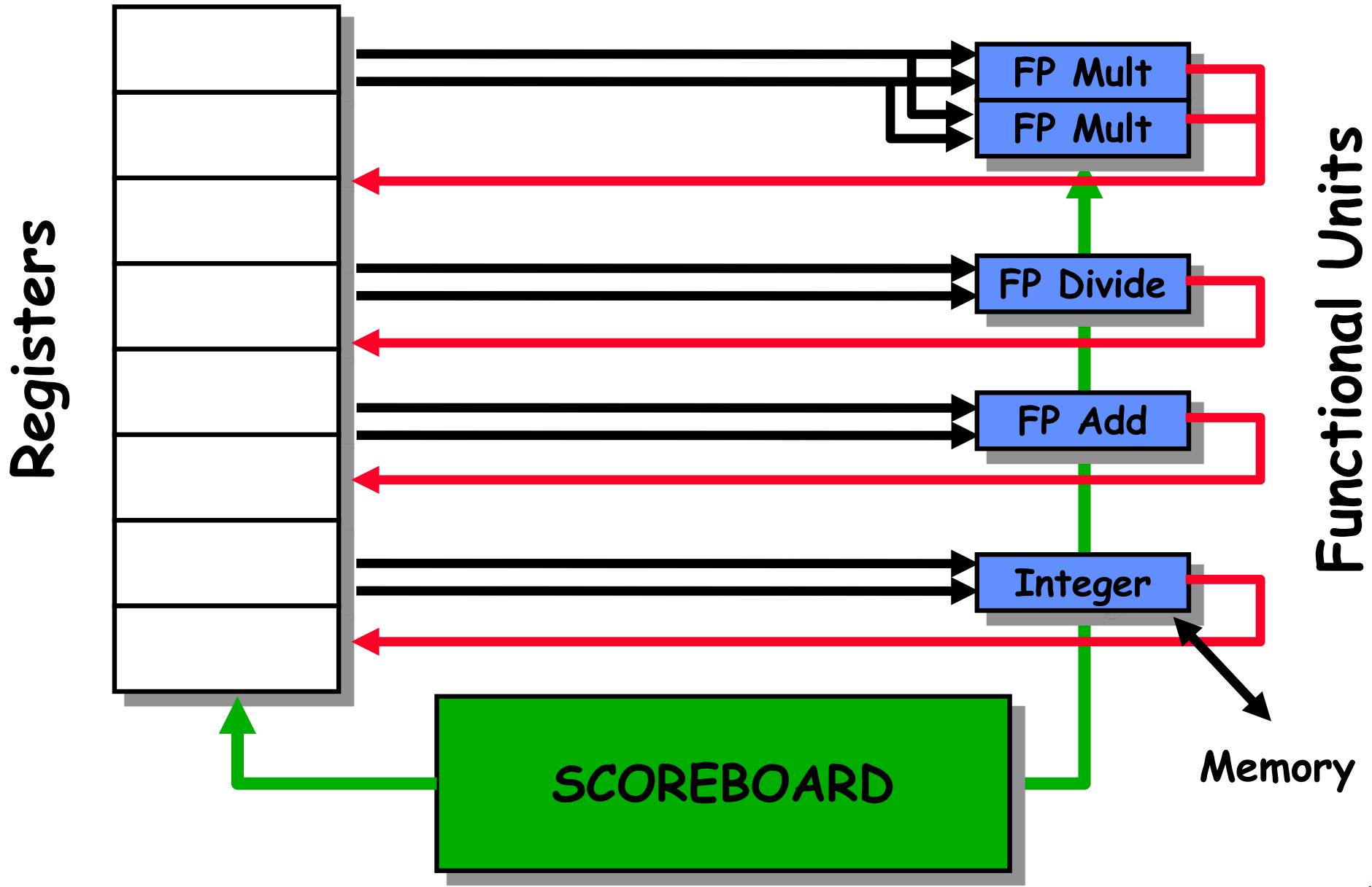


Tomasulo Algorithm

- For IBM 360/91 about 3 years after CDC 6600 (1966)
- Goal: High Performance without special compilers
- Differences between IBM 360 & CDC 6600 ISA
 - IBM has only 2 register specifiers/instr vs. 3 in CDC 6600
 - IBM has 4 FP registers vs. 8 in CDC 6600
 - IBM has memory-register ops
- Why Study? lead to Alpha 21264, HP 8000, MIPS 10000, Pentium II, PowerPC 604, ..., Today's processors

Organizations of Tomasulo's Algorithm

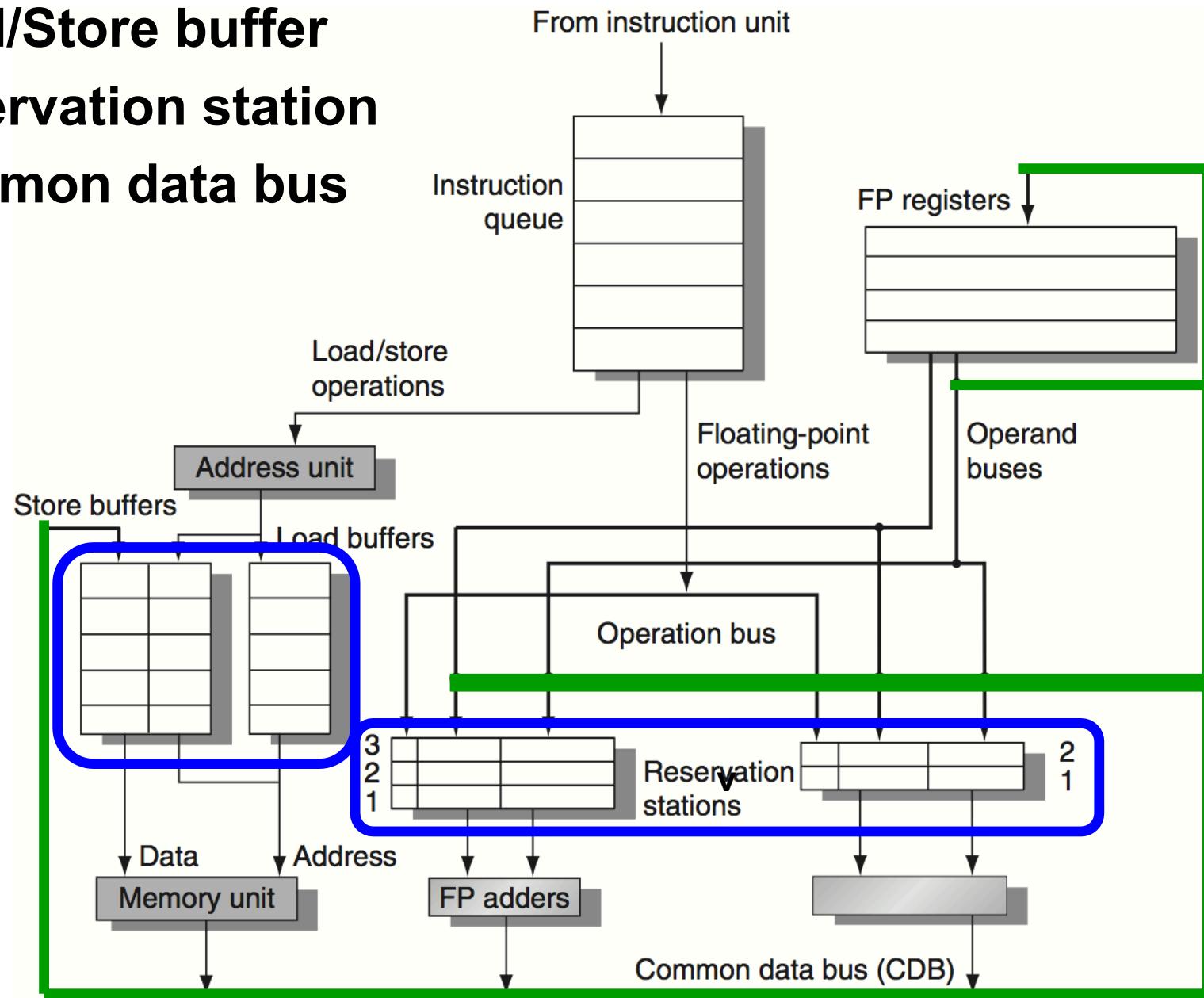- Load/Store buffer
- Reservation station
- Common data bus




Tomasulo Algorithm vs. Scoreboard

- Control & buffers **distributed** with Function Units (FU) vs. centralized in scoreboard;
 - FU buffers called “**reservation stations**”; have pending operands
- Registers in instructions replaced by values or pointers to reservation stations(RS); → **register renaming** ;
 - Avoids WAR, WAW hazards
 - More reservation stations than registers, so can do optimizations compilers can't
- Results to FU from RS, **not through registers**, over **Common Data Bus** that broadcasts results to all FUs
- Load and Stores treated as FUs with RSs as well
- Integer instructions can go past branches, allowing FP ops beyond basic block in FP queue

Register Renaming

- Register renaming by reservation stations (RS)

- Each entry contains:
 - » The instruction
 - » Buffered operand values (when available)
 - » Reservation station number of instruction providing the operand values
- RS fetches and buffers an operand as soon as it becomes available (not necessarily involving register file)
- Pending instructions designate the RS to which they will send their output
 - » Result values broadcast on the common data bus (CDB)
- Only the last output updates the register file
- As instructions are issued, the register specifiers are renamed with the reservation station
- May be more reservation stations than registers

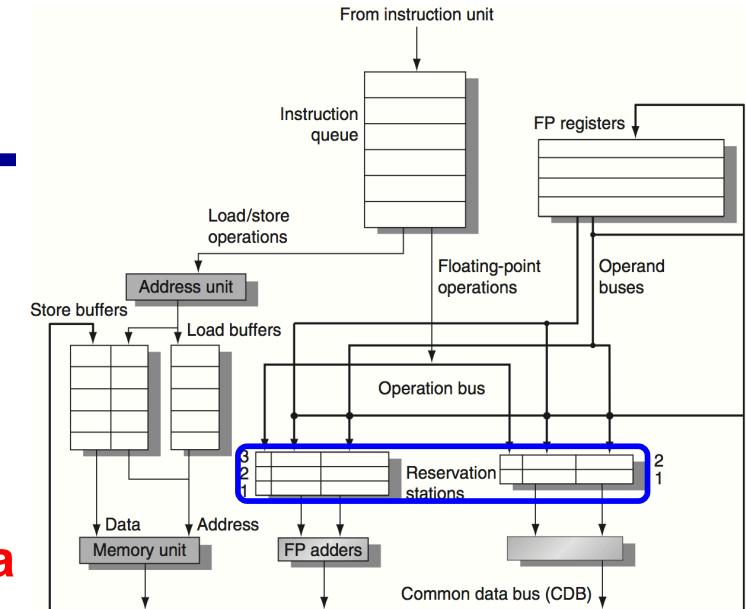

Reservation Station Components

Op: Operation to perform in the unit (e.g., + or -)

V_j, V_k: Value of Source operands

- Store buffers has V field, result to be stored

Q_j, Q_k: Reservation stations producing source registers (value to be written)

- Note: No ready flags as in Scoreboard; Q_j, Q_k=0 => ready in V_j or V_k
- Store buffers only have Q_i for RS producing result

Busy: Indicates reservation station or FU is busy

Q_i: Register result status—Indicates which functional unit will write each register, if one exists. Blank when no pending instructions that will write that register.

Three Stages of Tomasulo Algorithm

1. Issue—get instruction from FP Op Queue

If reservation station free (no structural hazard),
control issues instr & sends operands (renames registers).

2. Execution—operate on operands (EX)


When both operands ready then execute;
if not ready, watch Common Data Bus for result

3. Write result—finish execution (WB)

Write on Common Data Bus to all awaiting units;
mark reservation station available

- Normal data bus: data + destination (“go to” bus)
- Common data bus: data + source (“come from” bus)
 - 64 bits of data + 4 bits of Functional Unit source address
 - Write if matches expected Functional Unit (produces result)
 - Does the broadcast

Tomasulo Organization for the Example

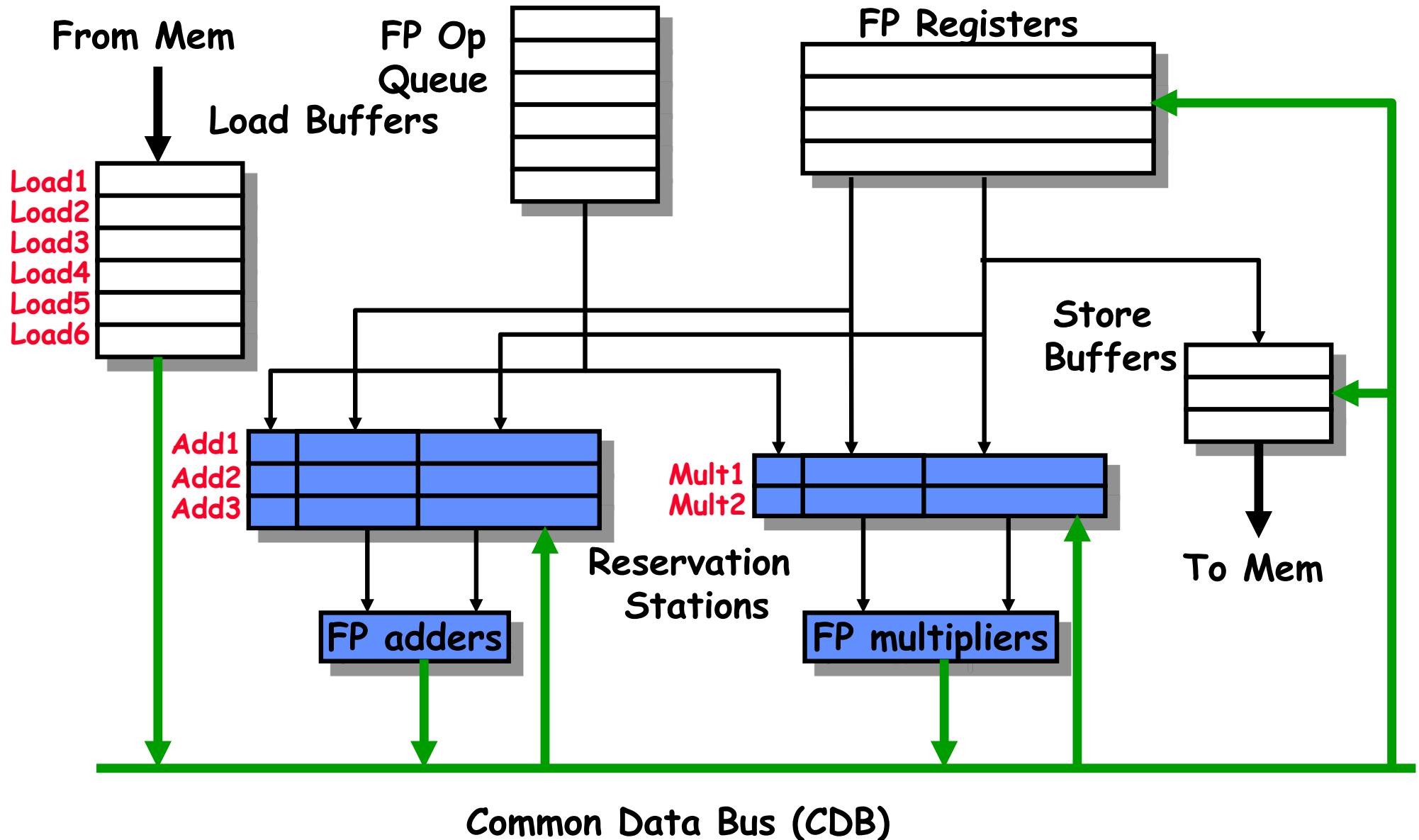

Tomasulo Example


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec Write		
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>
LD	F6	34+	R2		
LD	F2	45+	R3		
MULTD	F0	F2	F4		
SUBD	F8	F6	F2		
DIVD	F10	F0	F6		
ADDD	F6	F8	F2		

	Busy	Address
Load1	No	
Load2	No	
Load3	No	

Reservation Stations:

Time	Name	Busy	<i>S1</i>		<i>RS</i>	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
	Add2	No				
	Add3	No				
	Mult1	No				
	Mult2	No				

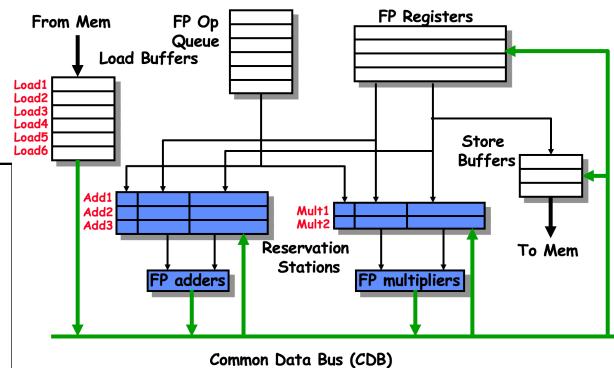

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
0	<i>FU</i>								

Tomasulo Example Cycle 1


Instruction status:

Instruction		<i>j</i>	<i>k</i>	<i>Issue</i>	<i>Exec</i>	<i>Write</i>
					<i>Comp</i>	<i>Result</i>
LD	F6	34+	R2	1		
LD	F2	45+	R3			
MULTD	F0	F2	F4			
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

	<i>Busy</i>	<i>Address</i>
Load1	Yes	34+R2
Load2	No	
Load3	No	

Reservation Stations:

<i>Time</i>	<i>Name</i>	<i>Busy</i>	<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>RS</i>	<i>RS</i>
	Add1	No					
	Add2	No					
	Add3	No					
	Mult1	No					
	Mult2	No					

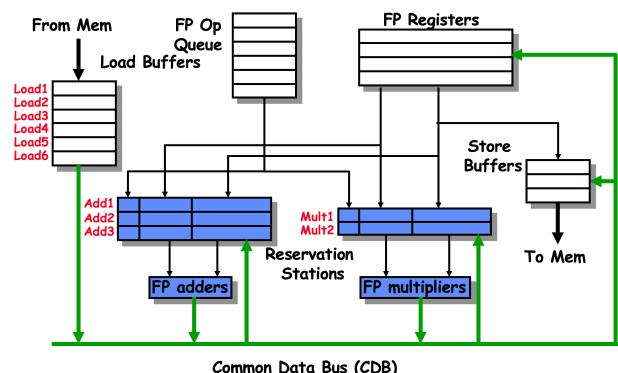

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>E6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
1					Load1				

Tomasulo Example Cycle 2


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec Write		
			Issue	Comp	Result
LD	F6	34+	R2	1	
LD	F2	45+	R3	2	
MULTD	F0	F2	F4		
SUBD	F8	F6	F2		
DIVD	F10	F0	F6		
ADDD	F6	F8	F2		

	Busy	Address
Load1	Yes	34+R2
Load2	Yes	45+R3
Load3	No	

Reservation Stations:

Time	Name	Busy	S1		RS		
			Op	Vj	Vk	Qj	Qk
	Add1	No					
	Add2	No					
	Add3	No					
	Mult1	No					
	Mult2	No					

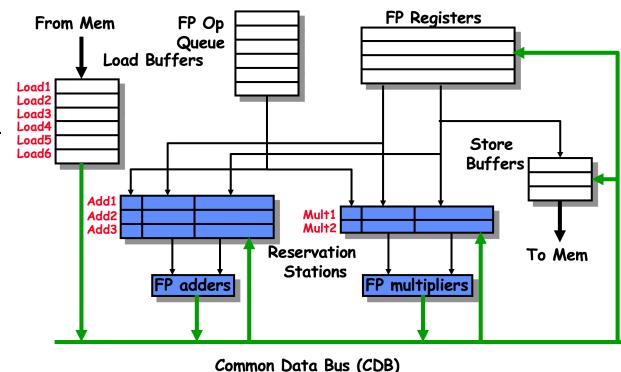

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
2		Load2		Load1					

Allow multiple outstanding loads


Tomasulo Example Cycle 3

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec Write			Busy	Address
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>		
LD	F6	34+	R2	1	3	Load1	Yes 34+R2
LD	F2	45+	R3	2		Load2	Yes 45+R3
MULTD	F0	F2	F4	3		Load3	No
SUBD	F8	F6	F2				
DIVD	F10	F0	F6				
ADDD	F6	F8	F2				

Reservation Stations:

Time	Name	Busy	S1		RS	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
	Add2	No				
	Add3	No				
	Mult1	Yes	MULTD		R(F4)	Load2
	Mult2	No				

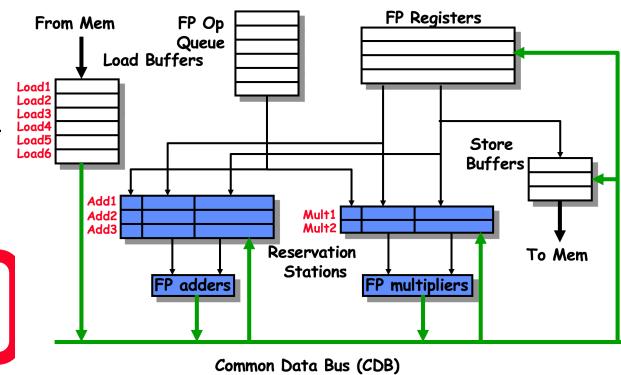

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
3	FU	Mult1	Load2		Load1				

- Note: registers names are removed ("renamed") in Reservation Stations; MULT issued vs. scoreboard
- Load1 completing; what is waiting for Load1?

Tomasulo Example Cycle 4

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write
			Issue	Comp	Result	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	
MULTD	F0	F2	F4	3		
SUBD	F8	F6	F2	4		
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

	Busy	Address
Load1	No	
Load2	Yes	45+R3
Load3	No	

Reservation Stations:

Time	Name	Busy	Op	<i>S1</i>	<i>S2</i>	<i>RS</i>	<i>RS</i>
				<i>V_j</i>	<i>V_k</i>	<i>Q_j</i>	<i>Q_k</i>
	Add1	Yes	SUBD	M(A1)			Load2
	Add2	No					
	Add3	No					
	Mult1	Yes	MULTD		R(F4)	Load2	
	Mult2	No					

Waiting for data from memory by the instruction originally in Load1

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
4	<i>FU</i>	Mult1	Load2	M(A1)	Add1				

- Load2 completing; what is waiting for Load2?

Tomasulo Example Cycle 5

Instruction status:

Instruction	<i>j</i>	<i>k</i>	<i>Issue</i>	<i>Exec</i>	<i>Write</i>	<i>Busy</i>	<i>Address</i>
				<i>Comp</i>	<i>Result</i>		
LD	F6	34+	R2	1	3	4	Load1 No
LD	F2	45+	R3	2	4	5	Load2 No
MULTD	F0	F2	F4	3			Load3 No
SUBD	F8	F6	F2	4			
DIVD	F10	F0	F6	5			
ADDD	F6	F8	F2				

Reservation Stations:

Time	Name	Busy	<i>Op</i>	<i>S1</i>	<i>S2</i>	<i>RS</i>	<i>RS</i>
				<i>Vj</i>	<i>Vk</i>	<i>Qj</i>	<i>Qk</i>
2	Add1	Yes	SUBD	M(A1)	M(A2)		
	Add2	No					
10	Add3	No					
	Mult1	Yes	MULTD	M(A2)	R(F4)		
	Mult2	Yes	DIVD			M(A1)	Mult1

Waiting for data from memory by the instruction originally in Load2

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
5	FU	Mult1	M(A2)		M(A1)	Add1	Mult2		

Tomasulo Example Cycle 6


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec Write		
			Issue	Comp	Result
LD	F6	34+	R2	1	3
LD	F2	45+	R3	2	4
MULTD	F0	F2	F4	3	
SUBD	F8	F6	F2	4	
DIVD	F10	F0	F6	5	
ADDD	F6	F8	F2	6	

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		S2		RS		RS	
			Op	Vj	Vk	Qj	Qk	Qj	Qk	Qj
1	Add1	Yes	SUBD	M(A1)	M(A2)					
	Add2	Yes	ADDD			M(A2)	Add1			
	Add3	No								
9	Mult1	Yes	MULTD	M(A2)	R(F4)					
	Mult2	Yes	DIVD		M(A1)	Mult1				

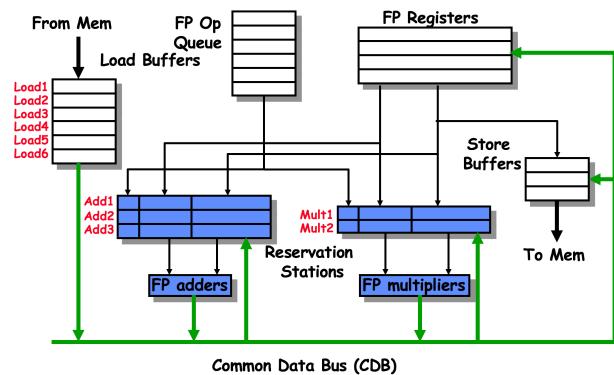

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
6	FU	Mult1	M(A2)		Add2	Add1	Mult2		

- Issue ADDD here vs. scoreboard?

Tomasulo Example Cycle 7


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec Write		
			Issue	Comp	Result
LD	F6	34+	R2	1	3
LD	F2	45+	R3	2	4
MULTD	F0	F2	F4	3	
SUBD	F8	F6	F2	4	7
DIVD	F10	F0	F6	5	
ADDD	F6	F8	F2	6	

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		S2		RS		RS	
			Op	Vj	Vk	Qj	Qk	Qj	Qk	Qj
0	Add1	Yes	SUBD	M(A1)	M(A2)					
	Add2	Yes	ADDD			M(A2)	Add1			
	Add3	No								
8	Mult1	Yes	MULTD	M(A2)	R(F4)					
	Mult2	Yes	DIVD		M(A1)	Mult1				

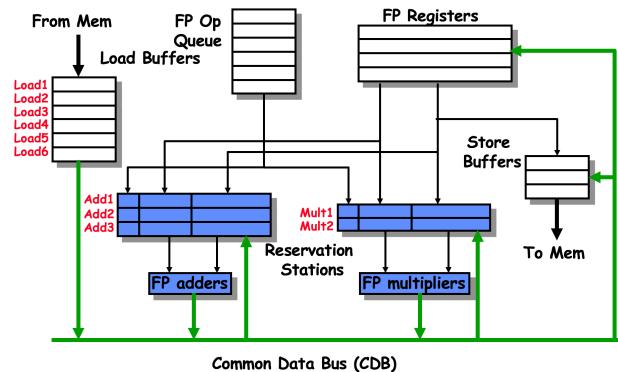

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
7	FU	Mult1	M(A2)		Add2	Add1	Mult2		

- Add1 completing; what is waiting for it?

Tomasulo Example Cycle 8


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	5
MULTD	F0	F2	F4	3		
SUBD	F8	F6	F2	4	7	8
DIVD	F10	F0	F6	5		
ADDD	F6	F8	F2	6		

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		S2		RS		RS	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>	<i>Qk</i>	<i>Qj</i>	<i>Qk</i>	
	Add1	No								
2	Add2	Yes	ADDD	(M-M)	M(A2)					
	Add3	No								
7	Mult1	Yes	MULTD	M(A2)	R(F4)					
	Mult2	Yes	DIVD		M(A1)	Mult1				

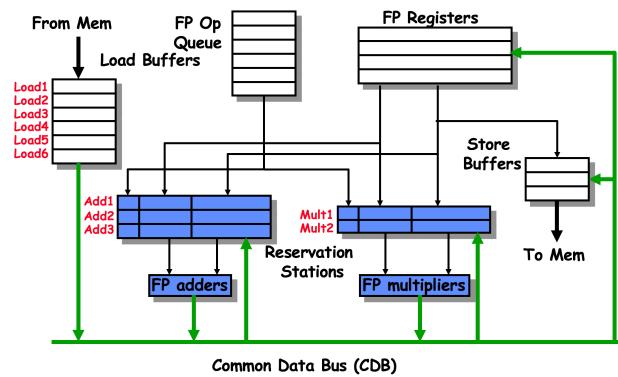

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
8	<i>FU</i>	Mult1	M(A2)		Add2	(M-M)	Mult2		

Tomasulo Example Cycle 9


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	5
MULTD	F0	F2	F4	3		
SUBD	F8	F6	F2	4	7	8
DIVD	F10	F0	F6	5		
ADDD	F6	F8	F2	6		

	Busy	Address
Load1	No	
Load2	No	
Load3	No	

Reservation Stations:

Time	Name	Busy	S1		RS	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
1	Add2	Yes	ADDD	(M-M)	M(A2)	
	Add3	No				
6	Mult1	Yes	MULTD	M(A2)	R(F4)	
	Mult2	Yes	DIVD		M(A1)	Mult1

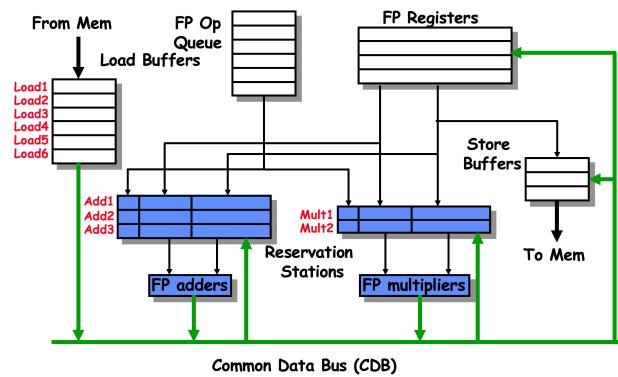

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
9	FU	Mult1	M(A2)		Add2	(M-M)	Mult2		

Tomasulo Example Cycle 10


Instruction status:

Instruction	<i>j</i>	<i>k</i>	<i>Issue</i>	<i>Exec</i>	<i>Write</i>
				<i>Comp</i>	<i>Result</i>
LD	F6	34+	R2	1	3
LD	F2	45+	R3	2	4
MULTD	F0	F2	F4	3	
SUBD	F8	F6	F2	4	7
DIVD	F10	F0	F6	5	
ADDD	F6	F8	F2	6	10

	<i>Busy</i>	<i>Address</i>
Load1	No	
Load2	No	
Load3	No	

Reservation Stations:

Time	Name	Busy	<i>Op</i>	<i>S1</i>	<i>S2</i>	<i>RS</i>	<i>RS</i>
				<i>Vj</i>	<i>Vk</i>	<i>Qj</i>	<i>Qk</i>
	Add1	No					
0	Add2	Yes	ADDD	(M-M)	M(A2)		
	Add3	No					
5	Mult1	Yes	MULTD	M(A2)	R(F4)		
	Mult2	Yes	DIVD		M(A1)	Mult1	

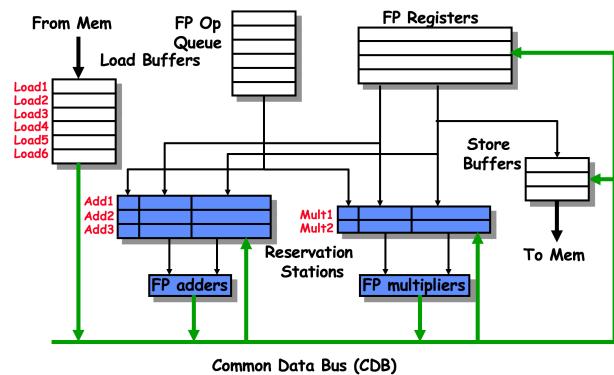

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
10	<i>FU</i>	Mult1	M(A2)		Add2	(M-M)	Mult2		

- Add2 completing; what is waiting for it?

Tomasulo Example Cycle 11


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec Write		
			Issue	Comp	Result
LD	F6	34+	R2	1	3
LD	F2	45+	R3	2	4
MULTD	F0	F2	F4	3	
SUBD	F8	F6	F2	4	7
DIVD	F10	F0	F6	5	
ADDD	F6	F8	F2	6	10
					11

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		RS	
			Op	<i>V_j</i>	<i>V_k</i>	<i>Q_j</i>
	Add1	No				
	Add2	No				
	Add3	No				
4	Mult1	Yes	MULTD	M(A2)	R(F4)	
	Mult2	Yes	DIVD		M(A1)	Mult1

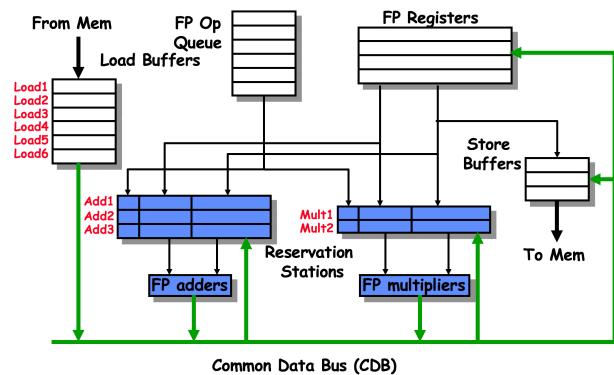

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
11	FU	Mult1	M(A2)	(M-M+N	(M-M)	Mult2			

- Write result of ADDD here vs. scoreboard?
- All quick instructions complete in this cycle!

Tomasulo Example Cycle 12


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write
			Issue	Comp	Result	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	5
MULTD	F0	F2	F4	3		
SUBD	F8	F6	F2	4	7	8
DIVD	F10	F0	F6	5		
ADDD	F6	F8	F2	6	10	11

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		S2		RS		RS	
			Op	<i>V_j</i>	<i>V_k</i>	<i>Q_j</i>	<i>Q_k</i>	<i>Q_j</i>	<i>Q_k</i>	
	Add1	No								
	Add2	No								
	Add3	No								
3	Mult1	Yes	MULTD	M(A2)	R(F4)					
	Mult2	Yes	DIVD		M(A1)	Mult1				

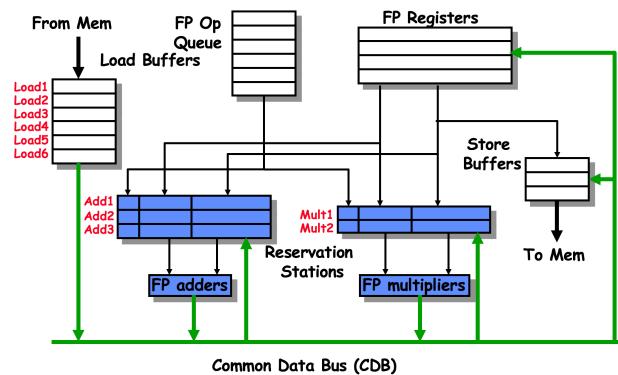

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
12	FU	Mult1	M(A2)	(M-M+M(M-M))	(M-M+M(M-M))	Mult2			

Tomasulo Example Cycle 13


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	5
MULTD	F0	F2	F4	3		
SUBD	F8	F6	F2	4	7	8
DIVD	F10	F0	F6	5		
ADDD	F6	F8	F2	6	10	11

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		RS	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
	Add2	No				
	Add3	No				
2	Mult1	Yes	MULTD	M(A2)	R(F4)	
	Mult2	Yes	DIVD		M(A1)	Mult1

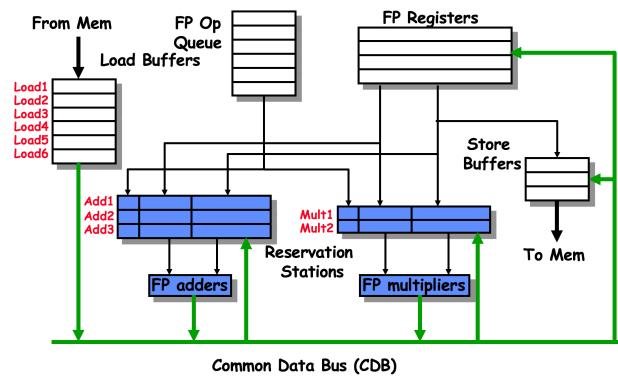

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
13	<i>FU</i>	Mult1	M(A2)		(M-M+M)(M-M)	Mult2			

Tomasulo Example Cycle 14


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	5
MULTD	F0	F2	F4	3		
SUBD	F8	F6	F2	4	7	8
DIVD	F10	F0	F6	5		
ADDD	F6	F8	F2	6	10	11

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		RS	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
	Add2	No				
	Add3	No				
1	Mult1	Yes	MULTD	M(A2)	R(F4)	
	Mult2	Yes	DIVD		M(A1)	Mult1

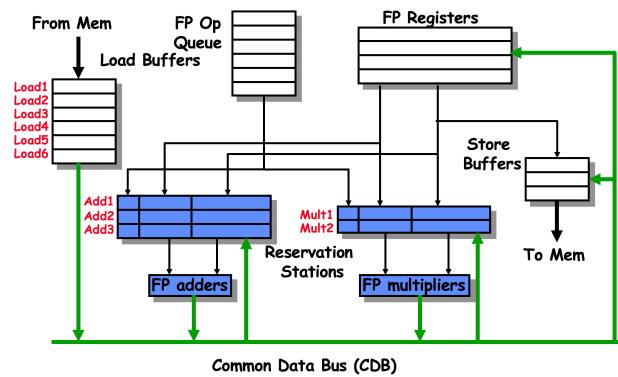

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
14	FU	Mult1	M(A2)	(M-M+M(M-M))	Mult2				

Tomasulo Example Cycle 15


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec Write		
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>
LD	F6	34+	R2	1	3 4
LD	F2	45+	R3	2	4 5
MULTD	F0	F2	F4	3	15
SUBD	F8	F6	F2	4	7 8
DIVD	F10	F0	F6	5	
ADDD	F6	F8	F2	6	10 11

	Busy	Address
Load1	No	
Load2	No	
Load3	No	

Reservation Stations:

Time	Name	Busy	S1		RS	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
	Add2	No				
	Add3	No				
0	Mult1	Yes	MULTD	M(A2)	R(F4)	
	Mult2	Yes	DIVD		M(A1)	Mult1

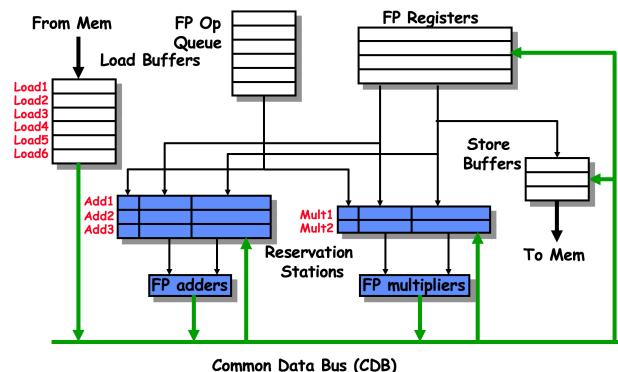

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
15	<i>FU</i>	Mult1	M(A2)		(M-M+M)(M-M)	Mult2			


Tomasulo Example Cycle 16

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write	Busy	Address
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>			
LD	F6	34+	R2	1	3	4	Load1	No
LD	F2	45+	R3	2	4	5	Load2	No
MULTD	F0	F2	F4	3	15	16	Load3	No
SUBD	F8	F6	F2	4	7	8		
DIVD	F10	F0	F6	5				
ADDD	F6	F8	F2	6	10	11		

Reservation Stations:

Time	Name	Busy	S1		S2		RS	
			Op	<i>V_j</i>	<i>V_k</i>	<i>Q_j</i>	<i>Q_k</i>	
	Add1	No						
	Add2	No						
	Add3	No						
	Mult1	No						
40	Mult2	Yes	DIVD	M*F4	M(A1)			

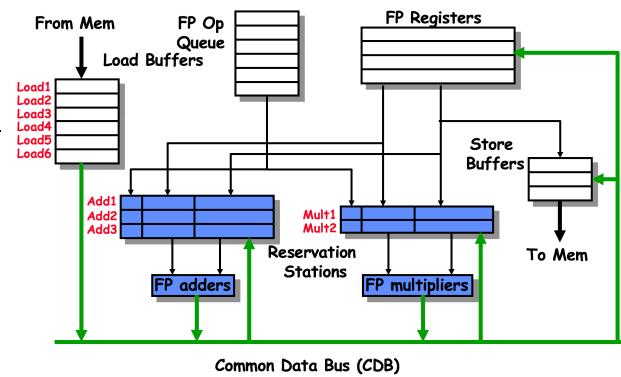

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
16	FU	M*F4	M(A2)	(M-M+M)(M-M)	Mult2				

**Faster than light computation
(skip a couple of cycles)**

Tomasulo Example Cycle 55


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			Write
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	5
MULTD	F0	F2	F4	3	15	16
SUBD	F8	F6	F2	4	7	8
DIVD	F10	F0	F6	5		
ADDD	F6	F8	F2	6	10	11

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	S1		RS	
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
	Add2	No				
	Add3	No				
	Mult1	No				
1	Mult2	Yes	DIVD	M*F4	M(A1)	

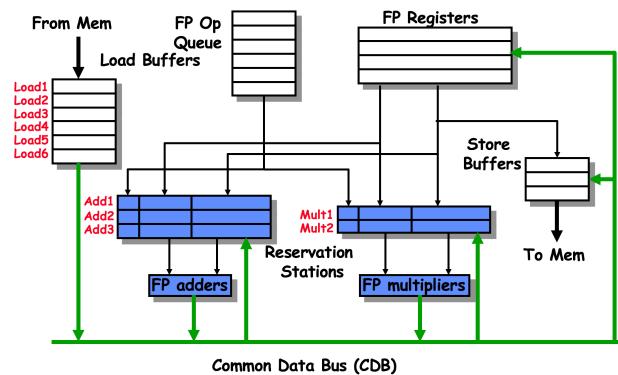

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
55	FU	M*F4	M(A2)	(M-M+M(M-M))	Mult2				

Tomasulo Example Cycle 56


Instruction status:

Instruction	<i>j</i>	<i>k</i>	<i>Issue</i>	<i>Exec</i>	<i>Write</i>
				<i>Comp</i>	<i>Result</i>
LD	F6	34+	R2	1	3
LD	F2	45+	R3	2	4
MULTD	F0	F2	F4	3	15
SUBD	F8	F6	F2	4	7
DIVD	F10	F0	F6	5	56
ADDD	F6	F8	F2	6	10
					11

	<i>Busy</i>	<i>Address</i>
Load1	No	
Load2	No	
Load3	No	

Reservation Stations:

Time	Name	<i>Busy</i>	<i>S1</i>	<i>S2</i>	<i>RS</i>	<i>RS</i>
			<i>Op</i>	<i>Vj</i>	<i>Vk</i>	<i>Qj</i>
	Add1	No				
	Add2	No				
	Add3	No				
	Mult1	No				
0	Mult2	Yes	DIVD	M*F4	M(A1)	

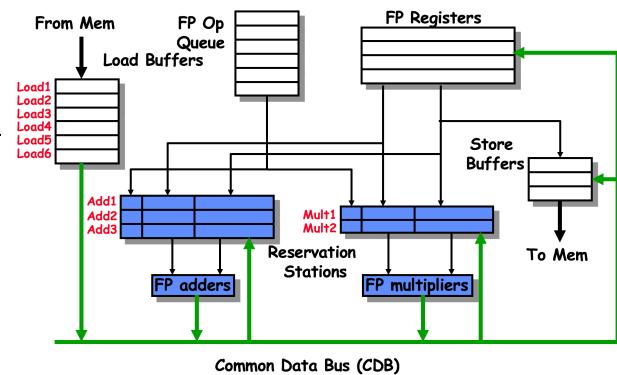

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
56	<i>FU</i>	M*F4	M(A2)		(M-M+M)	(M-M)	Mult2		

- Mult2 is completing; what is waiting for it?

Tomasulo Example Cycle 57


Instruction status:

Instruction	<i>j</i>	<i>k</i>	Exec			<i>Write</i>
			<i>Issue</i>	<i>Comp</i>	<i>Result</i>	
LD	F6	34+	R2	1	3	4
LD	F2	45+	R3	2	4	5
MULTD	F0	F2	F4	3	15	16
SUBD	F8	F6	F2	4	7	8
DIVD	F10	F0	F6	5	56	57
ADDD	F6	F8	F2	6	10	11

Busy	Address
Load1	No
Load2	No
Load3	No

Reservation Stations:

Time	Name	Busy	Op	<i>V_j</i>	<i>V_k</i>	<i>Q_j</i>	<i>Q_k</i>
	Add1	No					
	Add2	No					
	Add3	No					
	Mult1	No					
	Mult2	Yes	DIVD	M*F4	M(A1)		

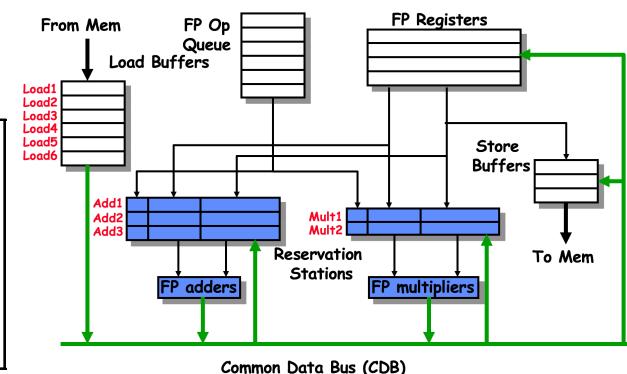

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
56	FU	M*F4	M(A2)	(M-M+M)(M-M)	Result				

- Once again: In-order issue, out-of-order execution and completion.

Compare to Scoreboard Cycle 62

Instruction status:

Instruction	j	k	Issue	Read	Exec	Write	Issue	Comp	Result	Exec	Write
				Oper	Comp	Result				Comp	Result
LD	F6	34+	R2	1	2	3	4			3	4
LD	F2	45+	R3	5	6	7	8			4	5
MULTD	F0	F2	F4	6	9	19	20	3	15	16	
SUBD	F8	F6	F2	7	9	11	12	4	7	8	
DIVD	F10	F0	F6	8	21	61	62	5	56	57	
ADDD	F6	F8	F2	13	14	16	22	6	10	11	

- Why take longer on scoreboard/6600?
 - Structural Hazards
 - Lack of forwarding

Tomasulo v. Scoreboard (IBM 360/91 v. CDC 6600)

Pipelined Functional Units	Multiple Functional Units
(6 load, 3 store, 3 +, 2 x/÷)	(1 load/store, 1 + , 2 x, 1 ÷)

window size: ≤ 14 instructions	≤ 5 instructions
---------------------------------------	-------------------------

No issue on structural hazard	same
WAR: renaming avoids	stall completion
WAW: renaming avoids	stall issue
Broadcast results from FU	Write/read registers
Control: reservation stations	central scoreboard

SUMMARY

Hardware Solution

- **Dynamic Scheduling**
 - Out-of-order execution and completion
- **Data Hazard via Register Renaming**
 - Dynamic RAW hazard detection and scheduling in data-flow fashion
 - Register renaming for WRA and WRA hazard (name conflict)
- **Implementations**
 - Scoreboard (CDC 6600 1963)
 - » Centralized register renaming
 - Tomasulo's Approach (IBM 360/91, 1966)
 - » Distributed control and renaming via reservation station, load/store buffer and common data bus (data+source)

Register Renaming Summary

- **Purpose of Renaming: removing “Anti-dependencies”**
 - Get rid of WAR and WAW hazards, since these are not “real” dependencies
- **Implicit Renaming: i.e. Tomasulo**
 - Registers changed into values or response tags
 - We call this “implicit” because space in register file may or may not be used by results!
- **Explicit Renaming: more physical registers than needed by ISA.**
 - Rename table: tracks current association between architectural registers and physical registers
 - Uses a translation table to perform compiler-like transformation on the fly
- **With Explicit Renaming:**
 - All registers concentrated in single register file
 - Can utilize bypass network that looks more like 5-stage pipeline
 - Introduces a register-allocation problem
 - » Need to handle branch misprediction and precise exceptions differently, but ultimately makes things simpler

Class Lecture Stops Here

TOMASULA LOOP EXAMPLE

Tomasulo Loop Example

Loop:	LD	F0	0	R1
	MULTD	F4	F0	F2
	SD	F4	0	R1
	SUBI	R1	R1	#8
	BNEZ	R1	Loop	

- Assume Multiply takes 4 clocks
- Assume first load takes 8 clocks (cache miss), second load takes 1 clock (hit)
- To be clear, will show clocks for SUBI, BNEZ
- Reality: integer instructions ahead

Loop Example

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1		Load1	No	
1	MULTD	F4	F0	F2		Load2	No	
1	SD	F4	0	R1		Load3	No	
2	LD	F0	0	R1		Store1	No	
2	MULTD	F4	F0	F2		Store2	No	
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	No					SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
0	80	Fu								

Loop Example Cycle 1

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2		Load2	No	
1	SD	F4	0	R1		Load3	No	
2	LD	F0	0	R1		Store1	No	
2	MULTD	F4	F0	F2		Store2	No	
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	No					SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
1	80	Fu	Load1							

Loop Example Cycle 2

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2	2	Load2	No	
1	SD	F4	0	R1		Load3	No	
2	LD	F0	0	R1		Store1	No	
2	MULTD	F4	F0	F2		Store2	No	
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	Yes	Multd		R(F4)	Load1	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
2	80	Fu	Load1		Mult1					

Loop Example Cycle 3

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2	2	Load2	No	
1	SD	F4	0	R1	3	Load3	No	
2	LD	F0	0	R1		Store1	Yes	80
2	MULTD	F4	F0	F2		Store2	No	Mult1
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	S1	S2	RS	Code:
				Vj	Vk	Qj	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	Yes	Multd				SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
3	80	Fu	Load1		Mult1					

- Implicit renaming sets up “DataFlow” graph

Loop Example Cycle 4

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2	2	Load2	No	
1	SD	F4	0	R1	3	Load3	No	
2	LD	F0	0	R1		Store1	Yes	80
2	MULTD	F4	F0	F2		Store2	No	Mult1
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	S1	S2	RS	Code:
				Vj	Vk	Qj	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	Yes	Multd		R(F4)	Load1	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
4	80	Fu	Load1		Mult1					

- Dispatching SUBI Instruction

Loop Example Cycle 5

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2	2	Load2	No	
1	SD	F4	0	R1	3	Load3	No	
2	LD	F0	0	R1		Store1	Yes	80
2	MULTD	F4	F0	F2		Store2	No	Mult1
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	RS		Code:
				S1	S2	
	Add1	No				LD F0 0 R1
	Add2	No				MULTD F4 F0 F2
	Add3	No				SD F4 0 R1
	Mult1	Yes	Multd	R(F4)	Load1	SUBI R1 R1 #8
	Mult2	No				BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
5	72	Fu	Load1		Mult1					

- And, BNEZ instruction

Loop Example Cycle 6

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2	2	Load2	Yes	72
1	SD	F4	0	R1	3	Load3	No	
2	LD	F0	0	R1	6	Store1	Yes	80
2	MULTD	F4	F0	F2		Store2	No	Mult1
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	Yes	Multd		R(F4)	Load1	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
6	72	Fu	Load2		Mult1					

- Notice that F0 never sees Load from location 80

Loop Example Cycle 7

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2	2	Load2	Yes	72
1	SD	F4	0	R1	3	Load3	No	
2	LD	F0	0	R1	6	Store1	Yes	80
2	MULTD	F4	F0	F2	7	Store2	No	Mult1
2	SD	F4	0	R1		Store3	No	

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	Yes	Multd		R(F2)	Load1	SUBI R1 R1 #8
	Mult2	Yes	Multd		R(F2)	Load2	BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
7	72	Fu	Load2		Mult2					

- Register file completely detached from computation
- First and Second iteration completely overlapped

Loop Example Cycle 8

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1	Load1	Yes	80
1	MULTD	F4	F0	F2	2	Load2	Yes	72
1	SD	F4	0	R1	3	Load3	No	
2	LD	F0	0	R1	6	Store1	Yes	80
2	MULTD	F4	F0	F2	7	Store2	Yes	72
2	SD	F4	0	R1	8	Store3	No	Mult2

Reservation Stations:

Time	Name	Busy	Op	S1 S2 RS			Code:	
				Vj	Vk	Qj	Qk	
	Add1	No						LD F0 0 R1
	Add2	No						MULTD F4 F0 F2
	Add3	No						SD F4 0 R1
	Mult1	Yes	Multd		R(F2)	Load1		SUBI R1 R1 #8
	Mult2	Yes	Multd		R(F2)	Load2		BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
8	72	Fu	Load2		Mult2					

Loop Example Cycle 9

Instruction status:

ITER	Instruction	j	k	Exec Write		Busy	Addr	Fu
				Issue	CompResult			
1	LD	F0	0	R1	1 9	Load1	Yes 80	
1	MULTD	F4	F0	F2	2	Load2	Yes 72	
1	SD	F4	0	R1	3	Load3	No	
2	LD	F0	0	R1	6	Store1	Yes 80	Mult1
2	MULTD	F4	F0	F2	7	Store2	Yes 72	Mult2
2	SD	F4	0	R1	8	Store3	No	

Reservation Stations:

Time	Name	Busy	Op	S1	S2	RS	Code:
				Vj	Vk	Qj	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	Yes Multd		R(F2)	Load1		SUBI R1 R1 #8
	Mult2	Yes Multd		R(F2)	Load2		BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
9	72	Fu	Load2		Mult2					

- Load1 completing: who is waiting?
- Note: Dispatching SUBI

Loop Example Cycle 10

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2			Load2	Yes 72
1	SD	F4	0	R1	3			Load3	No
2	LD	F0	0	R1	6	10		Store1	Yes 80 Mult1
2	MULTD	F4	F0	F2	7			Store2	Yes 72 Mult2
2	SD	F4	0	R1	8			Store3	No

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
4	Mult1	Yes	Multd M[80] R(F2)				SUBI R1 R1 #8
	Mult2	Yes	Multd	R(F2)	Load2		BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
10	64	Fu	Load2		Mult2					

- Load2 completing: who is waiting?
- Note: Dispatching BNEZ

Loop Example Cycle 11

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2			Load2	No
1	SD	F4	0	R1	3			Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 Mult1
2	MULTD	F4	F0	F2	7			Store2	Yes 72 Mult2
2	SD	F4	0	R1	8			Store3	No

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
3	Mult1	Yes	Multd M[80] R(F2)				SUBI R1 R1 #8
4	Mult2	Yes	Multd M[72] R(F2)				BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
11	64	Fu	Load3		Mult2					

- Next load in sequence

Loop Example Cycle 12

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2			Load2	No
1	SD	F4	0	R1	3			Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 Mult1
2	MULTD	F4	F0	F2	7			Store2	Yes 72 Mult2
2	SD	F4	0	R1	8			Store3	No

Reservation Stations:

Time	Name	Busy	Op	RS			Code:
				S1	S2	RS	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
2	Mult1	Yes	Multd M[80] R(F2)				SUBI R1 R1 #8
3	Mult2	Yes	Multd M[72] R(F2)				BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
12	64	Fu	Load3		Mult2					

- Why not issue third multiply?

Loop Example Cycle 13

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2			Load2	No
1	SD	F4	0	R1	3			Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 Mult1
2	MULTD	F4	F0	F2	7			Store2	Yes 72 Mult2
2	SD	F4	0	R1	8			Store3	No

Reservation Stations:

Time	Name	Busy	S1 S2 RS			Code:
			Op	Vj	Vk	
	Add1	No				LD F0 0 R1
	Add2	No				MULTD F4 F0 F2
	Add3	No				SD F4 0 R1
1	Mult1	Yes	Multd	M[80]	R(F2)	SUBI R1 R1 #8
2	Mult2	Yes	Multd	M[72]	R(F2)	BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
13	64	Fu	Load3		Mult2					

Loop Example Cycle 14

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2	14		Load2	No
1	SD	F4	0	R1	3			Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 Mult1
2	MULTD	F4	F0	F2	7			Store2	Yes 72 Mult2
2	SD	F4	0	R1	8			Store3	No

Reservation Stations:

Time	Name	Busy	Op	S1	S2	RS	Code:
				Vj	Vk	Qj	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
0	Mult1	Yes	Multd M[80] R(F2)				SUBI R1 R1 #8
1	Mult2	Yes	Multd M[72] R(F2)				BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
14	64	Fu	Load3		Mult2					

- Mult1 completing. Who is waiting?

Loop Example Cycle 15

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2	14	15	Load2	No
1	SD	F4	0	R1	3			Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 [80]*R2
2	MULTD	F4	F0	F2	7	15		Store2	Yes 72 Mult2
2	SD	F4	0	R1	8			Store3	No

Reservation Stations:

Time	Name	Busy	Op	S1	S2	RS	Code:
				Vj	Vk	Qj	
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	No					SUBI R1 R1 #8
0	Mult2	Yes	Multd M[72] R(F2)				BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
15	64	Fu	Load3		Mult2					

- Mult2 completing. Who is waiting?

Loop Example Cycle 16

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2	14	15	Load2	No
1	SD	F4	0	R1	3			Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 [80]*R2
2	MULTD	F4	F0	F2	7	15	16	Store2	Yes 72 [72]*R2
2	SD	F4	0	R1	8			Store3	No

Reservation Stations:

Time	Name	Busy	S1 S2 RS			Code:	
			Op	Vj	Vk		
	Add1	No				LD F0 0 R1	
	Add2	No				MULTD F4 F0 F2	
	Add3	No				SD F4 0 R1	
	Mult1	Yes	Multd		R(F2)	Load3	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
16	64	Fu	Load3		Mult1					

Loop Example Cycle 17

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2	14	15	Load2	No
1	SD	F4	0	R1	3			Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 [80]*R2
2	MULTD	F4	F0	F2	7	15	16	Store2	Yes 72 [72]*R2
2	SD	F4	0	R1	8			Store3	Yes 64 Mult1

Reservation Stations:

Time	Name	Busy	S1 S2 RS			Code:	
			Op	Vj	Vk		
	Add1	No				LD F0 0 R1	
	Add2	No				MULTD F4 F0 F2	
	Add3	No				SD F4 0 R1	
	Mult1	Yes	Multd		R(F2)	Load3	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
17	64	Fu	Load3		Mult1					

Loop Example Cycle 18

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2	14	15	Load2	No
1	SD	F4	0	R1	3	18		Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	Yes 80 [80]*R2
2	MULTD	F4	F0	F2	7	15	16	Store2	Yes 72 [72]*R2
2	SD	F4	0	R1	8			Store3	Yes 64 Mult1

Reservation Stations:

Time	Name	Busy	S1 S2 RS			Code:	
			Op	Vj	Vk		
	Add1	No				LD F0 0 R1	
	Add2	No				MULTD F4 F0 F2	
	Add3	No				SD F4 0 R1	
	Mult1	Yes	Multd		R(F2)	Load3	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
18	64	Fu	Load3		Mult1					

Loop Example Cycle 19

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2	14	15	Load2	No
1	SD	F4	0	R1	3	18	19	Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	No
2	MULTD	F4	F0	F2	7	15	16	Store2	Yes 72 [72]*R2
2	SD	F4	0	R1	8	19		Store3	Yes 64 Mult1

Reservation Stations:

Time	Name	Busy	SI			RS	Code:
			Op	Vj	Vk		
	Add1	No					LD F0 0 R1
	Add2	No					MULTD F4 F0 F2
	Add3	No					SD F4 0 R1
	Mult1	Yes	Multd		R(F2)	Load3	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
19	64	Fu	Load3		Mult1					

Loop Example Cycle 20

Instruction status:

ITER	Instruction	j	k	Exec Write			Busy	Addr	Fu
				Issue	Comp	Result			
1	LD	F0	0	R1	1	9	10	Load1	No
1	MULTD	F4	F0	F2	2	14	15	Load2	No
1	SD	F4	0	R1	3	18	19	Load3	Yes 64
2	LD	F0	0	R1	6	10	11	Store1	No
2	MULTD	F4	F0	F2	7	15	16	Store2	No
2	SD	F4	0	R1	8	19	20	Store3	Yes 64 Mult1

Reservation Stations:

Time	Name	Busy	S1 S2 RS			Code:	
			Op	Vj	Vk		
	Add1	No				LD F0 0 R1	
	Add2	No				MULTD F4 F0 F2	
	Add3	No				SD F4 0 R1	
	Mult1	Yes	Multd		R(F2)	Load3	SUBI R1 R1 #8
	Mult2	No					BNEZ R1 Loop

Register result status

Clock	R1	F0	F2	F4	F6	F8	F10	F12	...	F30
20	64	Fu	Load3		Mult1					

Why can Tomasulo overlap iterations of loops?

- **Register renaming**
 - Multiple iterations use different physical destinations for registers (dynamic loop unrolling).
- **Reservation stations**
 - Permit instruction issue to advance past integer control flow operations
- **Other idea: Tomasulo building dynamic “DataFlow” graph from instructions**
 - Fits in with readings for Wednesday

Summary


- **Scoreboard:** Track dependencies through reservations
 - Simple scheme for out-of-order execution
 - WAW and WAR hazards force stalls – cannot handle multiple instructions with same destination register
- **Reservations stations:** *renaming* to larger set of registers + buffering source operands
 - Prevents registers as bottleneck
 - Avoids WAR, WAW hazards of Scoreboard
 - Allows loop unrolling in HW
- **Dynamic hardware schemes** can unroll loops dynamically in hardware
 - Form of limited dataflow
 - Register renaming is essential
- **Lasting Contributions of Tomasulo Algorithm**
 - Dynamic scheduling
 - Register renaming
 - Load/store disambiguation
- **360/91 descendants are Pentium II; PowerPC 604; MIPS R10000; HP-PA 8000; Alpha 21264**

SCOREBOARD

Scoreboard: a bookkeeping technique

- Out-of-order execution divides ID stage:
 1. Issue—decode instructions, check for structural hazards
 2. Read operands—wait until no data hazards, then read operands
- Scoreboards date to CDC6600 in 1963
 - Readings for Monday include one on CDC6600
- Instructions execute whenever not dependent on previous instructions and no hazards.
- CDC 6600: In order issue, out-of-order execution, out-of-order commit (or completion)
 - No forwarding!
 - Imprecise interrupt/exception model for now

Scoreboard Architecture (CDC 6600)

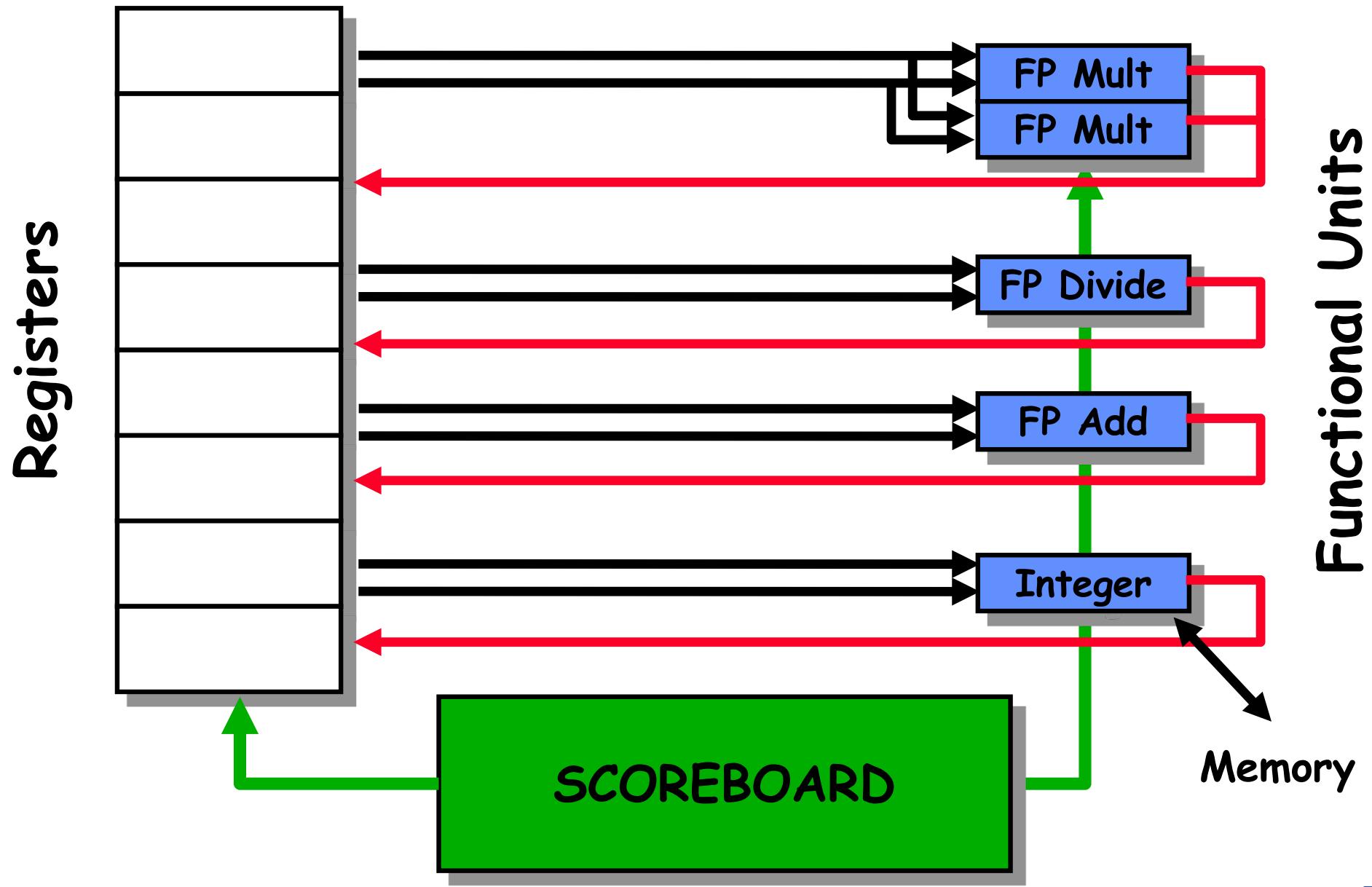

Scoreboard Implications

- Out-of-order completion => WAR, WAW hazards?
- Solutions for WAR:
 - Stall writeback until registers have been read
 - Read registers only during Read Operands stage
- Solution for WAW:
 - Detect hazard and stall issue of new instruction until other instruction completes
- No register renaming
- Need to have multiple instructions in execution phase => multiple execution units or pipelined execution units
- Scoreboard keeps track of dependencies between instructions that have already issued
- Scoreboard replaces ID, EX, WB with 4 stages

Four Stages of Scoreboard Control

- **Issue**—decode instructions & check for structural hazards (ID1)
 - Instructions issued in program order (for hazard checking)
 - Don't issue if structural hazard
 - Don't issue if instruction is output dependent on any previously issued but uncompleted instruction (no WAW hazards)
- **Read operands**—wait until no data hazards, then read operands (ID2)
 - All real dependencies (RAW hazards) resolved in this stage, since we wait for instructions to write back data.
 - No forwarding of data in this model!

Four Stages of Scoreboard Control

- **Execution**—operate on operands (EX)
 - The functional unit begins execution upon receiving operands. When the result is ready, it notifies the scoreboard that it has completed execution.
- **Write result**—finish execution (WB)
 - Stall until no WAR hazards with previous instructions:

Example:

DIVD	F0 , F2 , F4
ADDD	F10 , F0 , F8
SUBD	F8 , F8 , F14

CDC 6600 scoreboard would stall SUBD until ADDD reads operands

Three Parts of the Scoreboard

- **Instruction status:**
Which of 4 steps the instruction is in
- **Functional unit status:**—Indicates the state of the functional unit (FU). 9 fields for each functional unit
 - Busy:** Indicates whether the unit is busy or not
 - Op:** Operation to perform in the unit (e.g., + or -)
 - Fi:** Destination register
 - Fj,Fk:** Source-register numbers
 - Qj,Qk:** Functional units producing source registers Fj, Fk
 - Rj,Rk:** Flags indicating when Fj, Fk are ready
- **Register result status**—Indicates which functional unit will write each register, if one exists. Blank when no pending instructions will write that register

Scoreboard Example

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			<i>Issue</i>	<i>Oper</i>	<i>Comp</i>	<i>Result</i>
LD	F6	34+	R2			
LD	F2	45+	R3			
MULTD	F0	F2	F4			
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	Busy	Op	dest	<i>S1</i>	<i>S2</i>	<i>FU</i>	<i>FU</i>	<i>Fj?</i>	<i>Fk?</i>
				<i>Fi</i>	<i>Fj</i>	<i>Fk</i>	<i>Qj</i>	<i>Qk</i>	<i>Rj</i>	<i>Rk</i>
	Integer	No								
	Mult1	No								
	Mult2	No								
	Add	No								
	Divide	No								

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
<i>FU</i>									

Detailed Scoreboard Pipeline Control

Instruction status	Wait until	Bookkeeping
Issue	Not busy (FU) and not result(D)	$\text{Busy(FU)} \leftarrow \text{yes}; \text{Op(FU)} \leftarrow \text{op};$ $\text{Fi(FU)} \leftarrow 'D'; \text{Fj(FU)} \leftarrow 'S1';$ $\text{Fk(FU)} \leftarrow 'S2'; \text{Qj} \leftarrow \text{Result('S1')};$ $\text{Qk} \leftarrow \text{Result('S2')}; \text{Rj} \leftarrow \text{not Qj};$ $\text{Rk} \leftarrow \text{not Qk}; \text{Result('D')} \leftarrow \text{FU};$
Read operands	Rj and Rk	$\text{Rj} \leftarrow \text{No}; \text{Rk} \leftarrow \text{No}$
Execution complete	Functional unit done	
Write result	$\forall f ((\text{Fj}(f) \neq \text{Fi(FU)})$ $\text{or } \text{Rj}(f) = \text{No}) \text{ & }$ $(\text{Fk}(f) \neq \text{Fi(FU)} \text{ or }$ $\text{Rk}(f) = \text{No}))$	$\forall f (\text{if } \text{Qj}(f) = \text{FU} \text{ then } \text{Rj}(f) \leftarrow \text{Yes});$ $\forall f (\text{if } \text{Qk}(f) = \text{FU} \text{ then } \text{Rj}(f) \leftarrow \text{Yes});$ $\text{Result}(\text{Fi(FU)}) \leftarrow 0; \text{Busy(FU)} \leftarrow \text{No}$

Scoreboard Example: Cycle 1

Instruction status:

Instruction	j	k	Read	Exec		Write
				Issue	Oper	
LD	F6	34+	R2	1		
LD	F2	45+	R3			
MULTD	F0	F2	F4			
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	Busy	Op	dest	$S1$	$S2$	FU	FU	$Fj?$	$Fk?$
				F_i	F_j	F_k	Q_j	Q_k	R_j	R_k
	Integer	Yes	Load	F6		R2				Yes
	Mult1	No								
	Mult2	No								
	Add	No								
	Divide	No								

Register result status:

Clock	F_0	F_2	F_4	F_6	F_8	F_{10}	F_{12}	...	F_{30}
1									

Scoreboard Example: Cycle 2

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Issue	Read	Exec	Write
				Oper	Comp	Result
LD	F6	34+	R2	1	2	
LD	F2	45+	R3			
MULTD	F0	F2	F4			
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	Busy	Op	dest	<i>S1</i>	<i>S2</i>	<i>FU</i>	<i>FU</i>	<i>Fj?</i>	<i>Fk?</i>
				<i>Fi</i>	<i>Fj</i>	<i>Fk</i>	<i>Qj</i>	<i>Qk</i>	<i>Rj</i>	<i>Rk</i>
	Integer	Yes	Load	F6		R2				Yes
	Mult1	No								
	Mult2	No								
	Add	No								
	Divide	No								

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
2	<i>FU</i>								

- Issue 2nd LD?

Scoreboard Example: Cycle 3

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Issue	Read Open	Exec Comp	Write Result
			1	2	3	
LD	F6	34+	R2			
LD	F2	45+	R3			
MULTD	F0	F2	F4			
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	dest	S1	S2	FU	FU	Fj?	Fk?		
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	Yes	Load	F6		R2				No
	Mult1	No								
	Mult2	No								
	Add	No								
	Divide	No								

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
3	FU								

- Issue MULT?

Scoreboard Example: Cycle 4

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3
LD	F2	45+	R3			4
MULTD	F0	F2	F4			
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	dest		<i>S1</i>	<i>S2</i>	<i>FU</i>	<i>FU</i>	<i>Fj?</i>	<i>Fk?</i>
		<i>Busy</i>	<i>Op</i>	<i>F_i</i>	<i>F_j</i>	<i>F_k</i>	<i>Q_j</i>	<i>Q_k</i>	<i>R_j</i>
	Integer	No							
	Mult1	No							
	Mult2	No							
	Add	No							
	Divide	No							

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
4	<i>FU</i>								

Scoreboard Example: Cycle 5

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3
LD	F2	45+	R3	5		
MULTD	F0	F2	F4			
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	<i>F_i</i>	<i>F_j</i>	<i>F_k</i>	<i>Q_j</i>	<i>Q_k</i>	<i>R_j</i>
	Integer	Yes	Load	F2		R3			Yes
	Mult1	No							
	Mult2	No							
	Add	No							
	Divide	No							

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
5	FU	Integer							

Scoreboard Example: Cycle 6

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3
LD	F2	45+	R3	5	6	
MULTD	F0	F2	F4	6		
SUBD	F8	F6	F2			
DIVD	F10	F0	F6			
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj
	Integer	Yes	Load	F2		R3			Yes
	Mult1	Yes	Mult	F0	F2	F4	Integer		No Yes
	Mult2	No							
	Add	No							
	Divide	No							

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
6	FU	Mult1	Integer						

Scoreboard Example: Cycle 7

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write				
			Issue	Oper	Comp	Result	
LD	F6	34+	R2	1	2	3	4
LD	F2	45+	R3	5	6	7	
MULTD	F0	F2	F4	6			
SUBD	F8	F6	F2	7			
DIVD	F10	F0	F6				
ADDD	F6	F8	F2				

Functional unit status:

Time	Name	dest		<i>S1</i>	<i>S2</i>	<i>FU</i>	<i>FU</i>	<i>Fj?</i>	<i>Fk?</i>
		<i>Busy</i>	<i>Op</i>	<i>Fi</i>	<i>Fj</i>	<i>Fk</i>	<i>Qj</i>	<i>Qk</i>	<i>Rj</i>
	Integer	Yes	Load	F2		R3			No
	Mult1	Yes	Mult	F0	F2	F4	Integer		No Yes
	Mult2	No							
	Add	Yes	Sub	F8	F6	F2	Integer	Yes	No
	Divide	No							

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
7	<i>FU</i>	Mult1	Integer			Add			

- Read multiply operands?

Scoreboard Example: Cycle 8a

(First half of clock cycle)

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write				
			Issue	Oper	Comp	Result	
LD	F6	34+	R2	1	2	3	4
LD	F2	45+	R3	5	6	7	
MULTD	F0	F2	F4	6			
SUBD	F8	F6	F2	7			
DIVD	F10	F0	F6	8			
ADDD	F6	F8	F2				

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	<i>Fi</i>	<i>Fj</i>	<i>Fk</i>	<i>Qj</i>	<i>Qk</i>	<i>Rj</i>
	Integer	Yes	Load	F2		R3			No
	Mult1	Yes	Mult	F0	F2	F4	Integer		No Yes
	Mult2	No							
	Add	Yes	Sub	F8	F6	F2	Integer	Yes	No
	Divide	Yes	Div	F10	F0	F6	Mult1	No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
8	FU	Mult1	Integer		Add	Divide			

Scoreboard Example: Cycle 8b (Second half of clock cycle)

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write				
			Issue	Oper	Comp	Result	
LD	F6	34+	R2	1	2	3	4
LD	F2	45+	R3	5	6	7	8
MULTD	F0	F2	F4	6			
SUBD	F8	F6	F2	7			
DIVD	F10	F0	F6	8			
ADDD	F6	F8	F2				

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	<i>Fi</i>	<i>Fj</i>	<i>Fk</i>	<i>Qj</i>	<i>Qk</i>	<i>Rj</i>
	Integer	No							
	Mult1	Yes	Mult	F0	F2	F4		Yes	Yes
	Mult2	No							
	Add	Yes	Sub	F8	F6	F2		Yes	Yes
	Divide	Yes	Div	F10	F0	F6	Mult1	No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
8	FU	Mult1			Add	Divide			

Scoreboard Example: Cycle 9

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	<i>Fi</i>	<i>Fj</i>	<i>Fk</i>	<i>Qj</i>	<i>Qk</i>	<i>Rj</i>
	Integer	No							
10	Mult1	Yes	Mult	F0	F2	F4		Yes	Yes
	Mult2	No							
2	Add	Yes	Sub	F8	F6	F2		Yes	Yes
	Divide	Yes	Div	F10	F0	F6	Mult1	No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
9	FU	Mult1			Add	Divide			

- Read operands for MULT & SUB? Issue ADDD?

Scoreboard Example: Cycle 10

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	Busy	Op	dest	S1	S2	FU	FU	Fj?	Fk?
				Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
9	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
1	Add	Yes	Sub	F8	F6	F2			No	No
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
10	FU	Mult1			Add	Divide			

Scoreboard Example: Cycle 11

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	Busy	Op	dest	S1	S2	FU	FU	Fj?	Fk?
				Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
8	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
0	Add	Yes	Sub	F8	F6	F2			No	No
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
11	FU	Mult1			Add	Divide			

Scoreboard Example: Cycle 12

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2			

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?	
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
7	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
	Add	No								
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock		F0	F2	F4	F6	F8	F10	F12	...	F30
12	FU	Mult1						Divide		

- **Read operands for DIVD?**

Scoreboard Example: Cycle 13

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2	13		

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?	
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
6	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
	Add	Yes	Add	F6	F8	F2			Yes	Yes
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
13	FU	Mult1		Add		Divide			

Scoreboard Example: Cycle 14

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2	13	14	

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?	
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
5	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
2	Add	Yes	Add	F6	F8	F2			Yes	Yes
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
14	FU	Mult1			Add		Divide		

Scoreboard Example: Cycle 15

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2	13	14	

Functional unit status:

Time	Name	Busy	dest		S1	S2	FU	FU	Fj?	Fk?
			Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
4	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
1	Add	Yes	Add	F6	F8	F2			No	No
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
15	FU	Mult1			Add		Divide		

Scoreboard Example: Cycle 16

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2	13	14	16

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?	
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
3	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
0	Add	Yes	Add	F6	F8	F2			No	No
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
16	FU	Mult1		Add		Divide			

Scoreboard Example: Cycle 17

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2	13	14	16

WAR Hazard!

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?	
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
2	Mult1	Yes	Mult	F0	F2	F4		No	No	
	Mult2	No								
	Add	Yes	Add	F6	F8	F2		No	No	
	Divide	Yes	Div	F10	F0	F6	mult1	No	Yes	

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
17	FU	Mult1			Add				Divide

- Why not write result of ADD???

Scoreboard Example: Cycle 18

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2	13	14	16

Functional unit status:

Time	Name	Busy	dest		S1	S2	FU	FU	Fj?	Fk?
			Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
1	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
	Add	Yes	Add	F6	F8	F2			No	No
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
18	FU	Mult1		Add		Divide			

Scoreboard Example: Cycle 19

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	19
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8		
ADDD	F6	F8	F2	13	14	16

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?	
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
0	Mult1	Yes	Mult	F0	F2	F4			No	No
	Mult2	No								
	Add	Yes	Add	F6	F8	F2			No	No
	Divide	Yes	Div	F10	F0	F6	Mult1		No	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
19	FU	Mult1		Add		Divide			

Scoreboard Example: Cycle 20

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write				
			Issue	Oper	Comp	Result	
LD	F6	34+	R2	1	2	3	4
LD	F2	45+	R3	5	6	7	8
MULTD	F0	F2	F4	6	9	19	20
SUBD	F8	F6	F2	7	9	11	12
DIVD	F10	F0	F6	8			
ADDD	F6	F8	F2	13	14	16	

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj
	Integer	No							
	Mult1	No							
	Mult2	No							
	Add	Yes	Add	F6	F8	F2		No	No
	Divide	Yes	Div	F10	F0	F6		Yes	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
20	FU				Add		Divide		

Scoreboard Example: Cycle 21

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	19 20
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8	21	
ADDD	F6	F8	F2	13	14	16

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj
	Integer	No							
	Mult1	No							
	Mult2	No							
	Add	Yes	Add	F6	F8	F2		No	No
	Divide	Yes	Div	F10	F0	F6		Yes	Yes

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
21	FU				Add		Divide		

- WAR Hazard is now gone...

Scoreboard Example: Cycle 22

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write			
			Issue	Oper	Comp	Result
LD	F6	34+	R2	1	2	3 4
LD	F2	45+	R3	5	6	7 8
MULTD	F0	F2	F4	6	9	19 20
SUBD	F8	F6	F2	7	9	11 12
DIVD	F10	F0	F6	8	21	
ADDD	F6	F8	F2	13	14	16 22

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj
	Integer	No							
	Mult1	No							
	Mult2	No							
	Add	No							
39	Divide	Yes	Div	F10	F0	F6		No	No

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
22	FU								Divide

**Faster than light computation
(skip a couple of cycles)**

Scoreboard Example: Cycle 61

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write				
			Issue	Oper	Comp	Result	
LD	F6	34+	R2	1	2	3	4
LD	F2	45+	R3	5	6	7	8
MULTD	F0	F2	F4	6	9	19	20
SUBD	F8	F6	F2	7	9	11	12
DIVD	F10	F0	F6	8	21	61	
ADDD	F6	F8	F2	13	14	16	22

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj
	Integer	No							
	Mult1	No							
	Mult2	No							
	Add	No							
0	Divide	Yes	Div	F10	F0	F6		No	No

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
61	FU								Divide

Scoreboard Example: Cycle 62

Instruction status:

Instruction	<i>j</i>	<i>k</i>	Read Exec Write				
			Issue	Oper	Comp	Result	
LD	F6	34+	R2	1	2	3	4
LD	F2	45+	R3	5	6	7	8
MULTD	F0	F2	F4	6	9	19	20
SUBD	F8	F6	F2	7	9	11	12
DIVD	F10	F0	F6	8	21	61	62
ADDD	F6	F8	F2	13	14	16	22

Functional unit status:

Time	Name	dest		S1	S2	FU	FU	Fj?	Fk?	
		Busy	Op	Fi	Fj	Fk	Qj	Qk	Rj	Rk
	Integer	No								
	Mult1	No								
	Mult2	No								
	Add	No								
	Divide	No								

Register result status:

Clock	F0	F2	F4	F6	F8	F10	F12	...	F30
62	FU								

Review: Scoreboard Example: Cycle 62

Instruction status:

Instruction	<i>j</i>	<i>k</i>	<i>Issue</i>	Read	Exec	Write
				<i>Oper</i>	<i>Comp</i>	<i>Result</i>
LD	F6	34+	R2	1	2	3
LD	F2	45+	R3	5	6	7
MULTD	F0	F2	F4	6	9	19
SUBD	F8	F6	F2	7	9	11
DIVD	F10	F0	F6	8	21	61
ADDD	F6	F8	F2	13	14	16

Functional unit status:

Time	Name	dest	<i>S1</i>	<i>S2</i>	<i>FU</i>	<i>FU</i>	<i>Fj?</i>	<i>Fk?</i>
		<i>Busy</i>	<i>Op</i>	<i>Fi</i>	<i>Fj</i>	<i>Fk</i>	<i>Qj</i>	<i>Qk</i>
	Integer	No						
	Mult1	No						
	Mult2	No						
	Add	No						
	Divide	No						

Register result status:

Clock	<i>F0</i>	<i>F2</i>	<i>F4</i>	<i>F6</i>	<i>F8</i>	<i>F10</i>	<i>F12</i>	...	<i>F30</i>
62	<i>FU</i>								

- In-order issue; out-of-order execute & commit

CDC 6600 Scoreboard

- Speedup 1.7 from compiler; 2.5 by hand
BUT slow memory (no cache) limits benefit
- Limitations of 6600 scoreboard:
 - No forwarding hardware
 - Limited to instructions in basic block (small *window*)
 - Small number of functional units (structural hazards), especially integer/load store units
 - Do not issue on structural hazards
 - Wait for WAR hazards
 - Prevent WAW hazards

A Useful Slide

- Interesting Resource: <http://bitsavers.org>
 - Has digital versions of users manuals for old machines
 - Quite interesting!
 - I'll link in some of them to your reading pages when it is appropriate
 - Very limited bandwidth: use mirrors such as:
<http://bitsavers.vt100.net>